

TIMER ON PROGRAMMING EXAMPLE

These are examples of the different ways a Timer ON instruction can be programmed into a rung or network.

The two formats are **Timer On Delay On** and **Timer On Delay Off**.



Timer On Delay On after the Timer completes elapsing, timed out, the output controlled is turned On.

Timer On Delay Off while the timer is elapsing the controlled output is On. When the timer completes elapsing, timed out, the controlled output turns Off.



Notice the **Timer On Delay On** use the instruction type **-] [-** with the **.DN** or **.Q** timer status bit to control the output and the **Timer On Delay Off** uses the **-]/[-** instruction type.

STUDIO 5000 EXAMPLES


TIMER ON DELAY ON (Energize to Delay On)

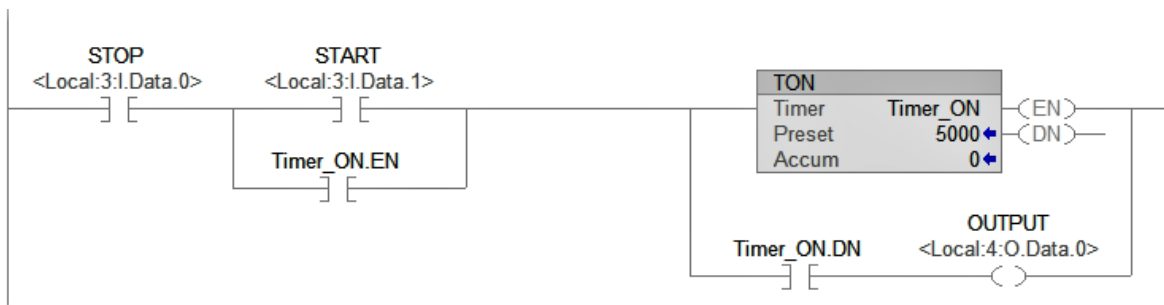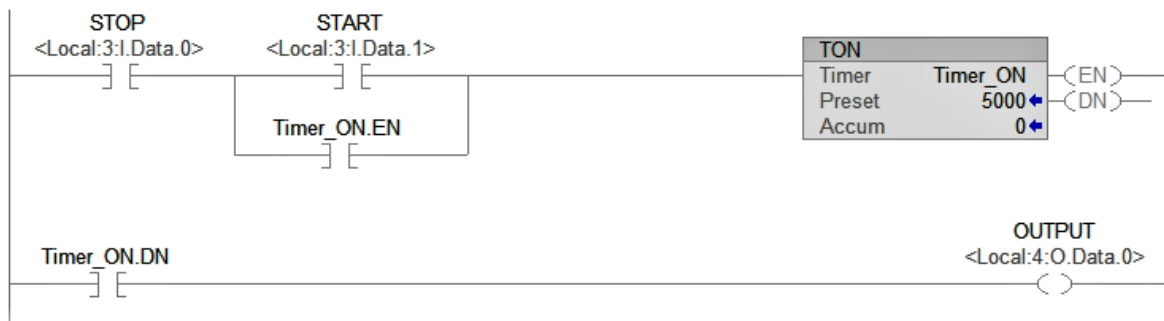

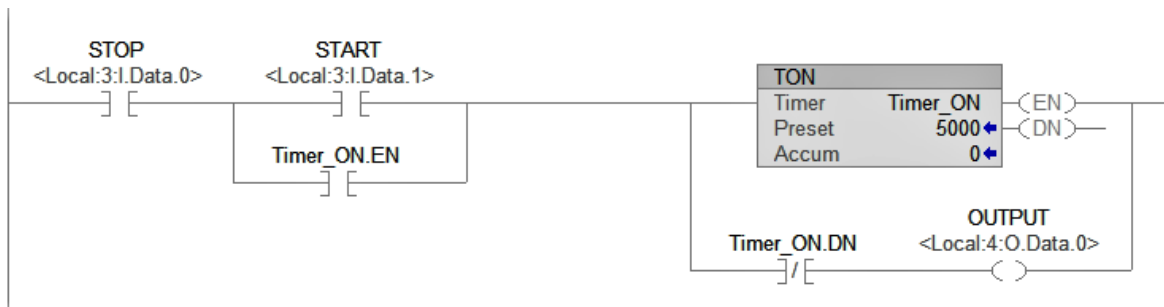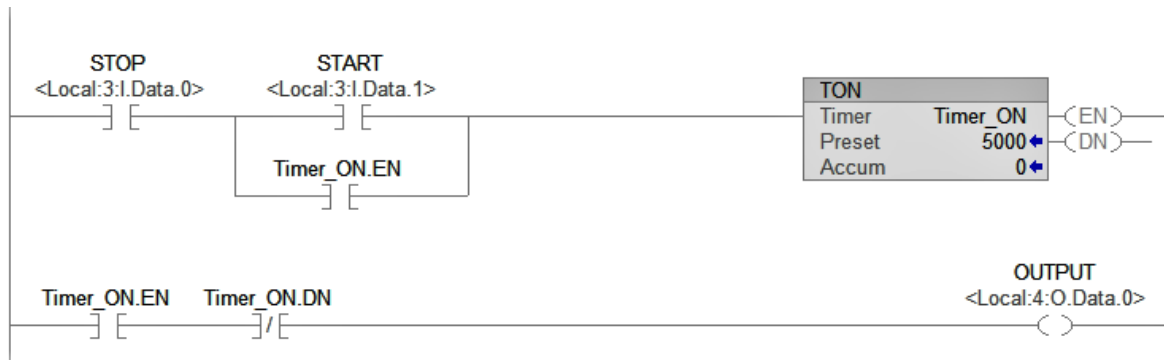TIMER ON DELAY OFF (Energize to Delay Off)




TIMER ON TIMER TIMING

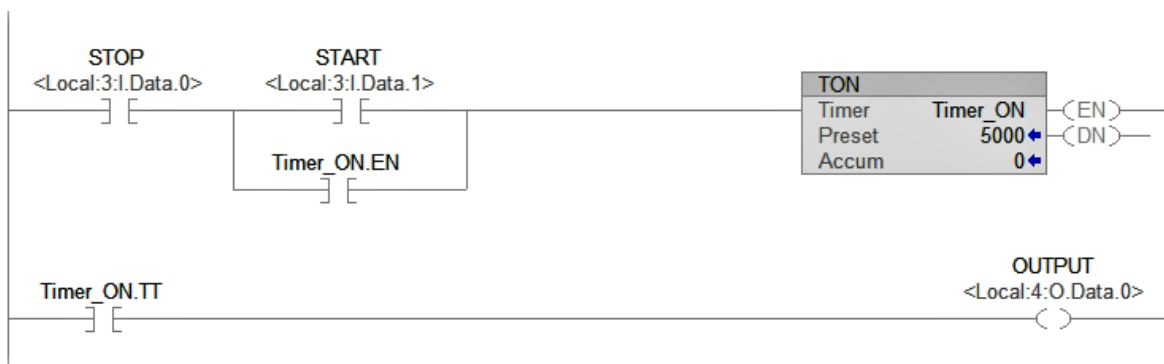

SIEMENS TIMER EXAMPLES

TIMER ON DELAY ON (Energize to Delay On)

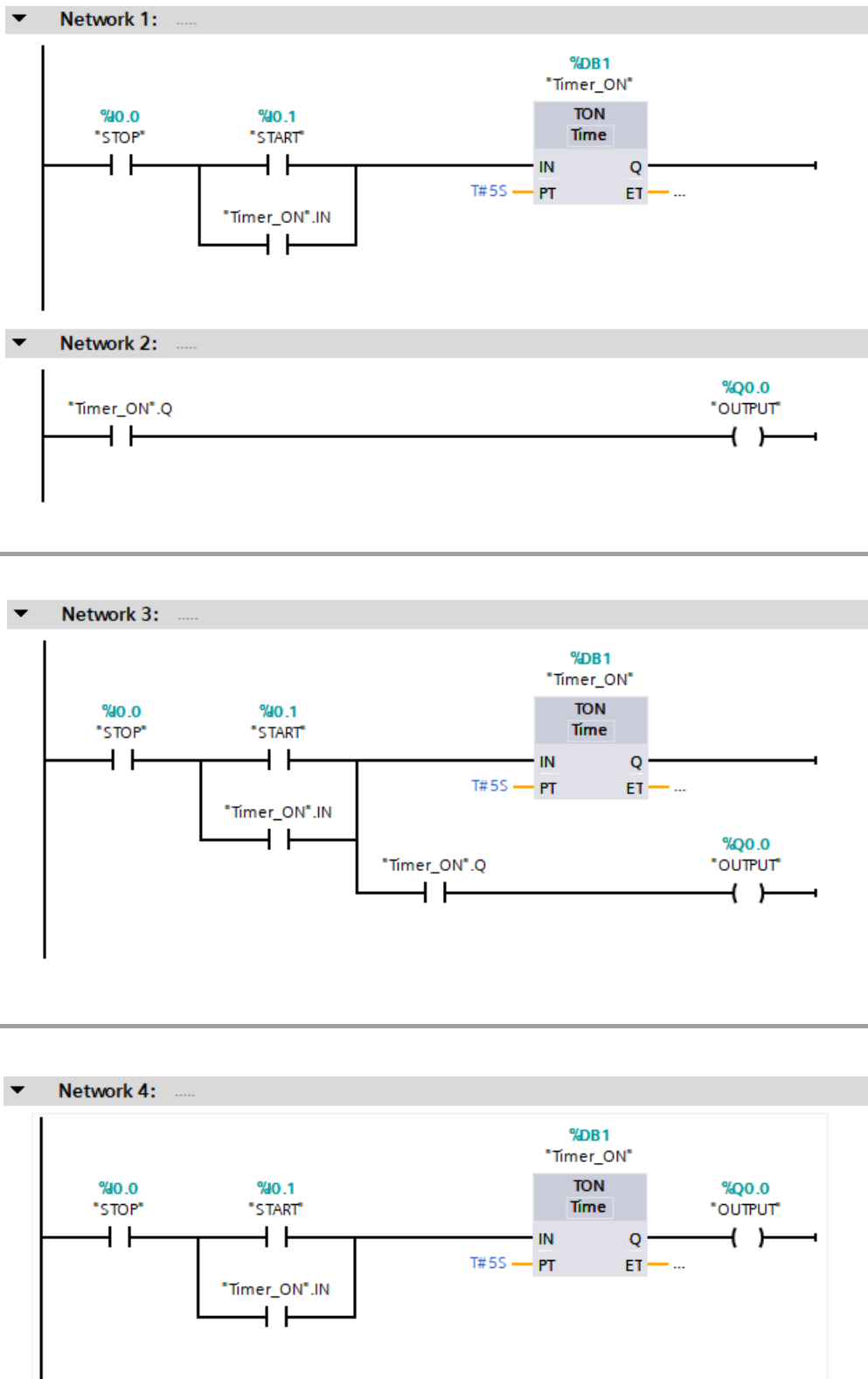

TIMER ON DELAY OFF (Energize to Delay Off)

