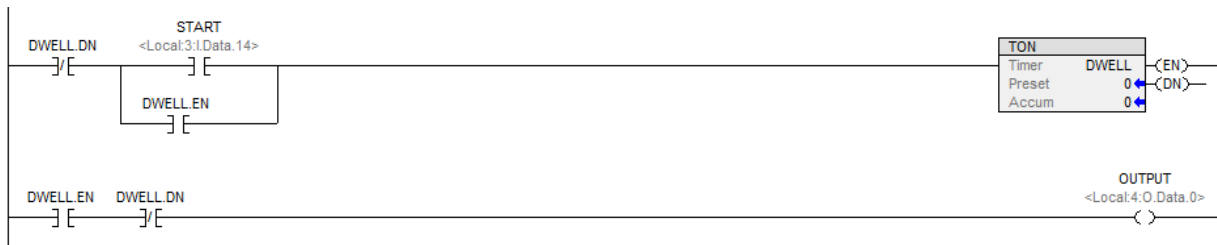



NOTE: This examples are for the MOVE lab.
For the DISPENSE Final the DWELL.DN breaking the holding circuit or controlling the output are replaced with the Low Level Float Switch.

MOVE TIMER RUNG EXAMPLES STUDIO 5000

The following three examples are variations of the “conventional” logic structures.





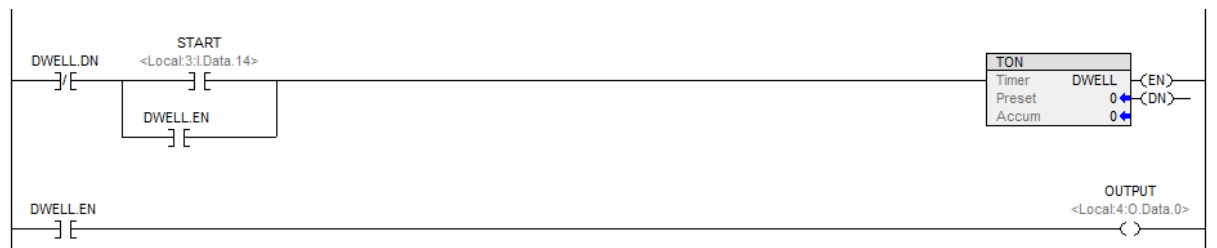The following two examples are valid because the Timer resets itself and results in the Output turning off.



MOVE TIMER RUNG EXAMPLES STUDIO SIEMENS

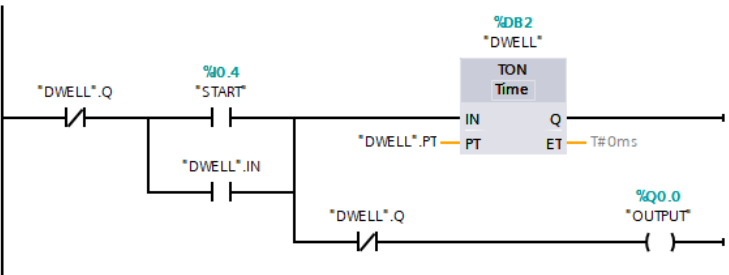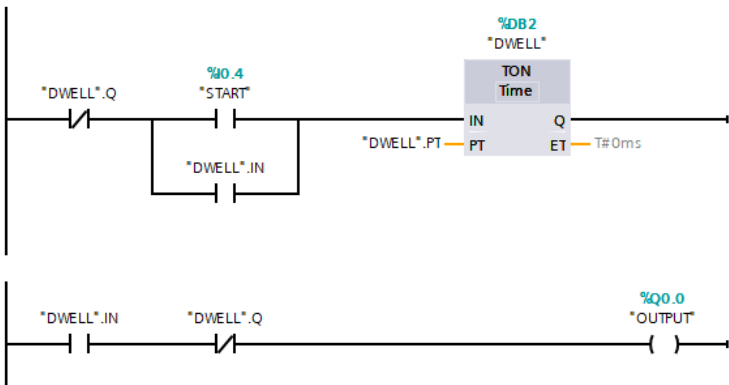The following two examples are variations of the “conventional” logic structures.



The following two examples are valid because the Timer resets itself and results in the Output turning off.

